

ECE 337: ASIC Design

Lab 6

UART: A Generic Asynchronous Serial Interface

Week 6

Deadlines & Reminders

- Lab 6 Deadlines
 - Required Preparation Phase (Design planning)
 - Due by Late Night two days before your lab 7 (Week 7)
 - Example: Late Sunday Night for Tuesday Lab Sections
 - Automated Design Grading
 - Due by start of your lab 7 (Week 7)
- Submission Notes
 - Must achieve 50% on latest mapped grading to pass the lab
 - Top level port names and module names must be IDENTICAL to what is listed in the manual or your submission attempt will be wasted.
- Check prior scores & attempts used
 - Submit Lab6 -c

What is a UART?

- A general purpose serial communication interface.
 - Uses: computer serial ports, USB interfaces, most modems, infrared, and wireless interfaces.
 - Why? Lets you use one wire or channel for each direction.

Why Study UART Design?

- Serial interfaces are a very common pieces of ASIC and processor designs
 - Minimize pins on packaging
 - Minimizes packaging costs
 - Minimizes packaged chip size
 - Enable standard pin interfaces for a variety of ASICs


In lab

- Completing the design of a receiver portion of a UART
 - Universal Asynchronous Receiver Transmitter
 - Given most pieces of the design
 - Only have to make the sr_9bit, controller, timer, and top-level blocks
 - Hint – the timer is just a counter or chain of counters
 - Given a starter test bench

Major functions of a UART

- Receiver Block
 - Receives serial data, stores in parallel to register
 - Register is read by an external device
- Transmitter Block
 - External device loads data in parallel into register
 - Serially transmit the data
- Data is transmitted/received one byte at a time
 - Each byte handled separately

Top Level View

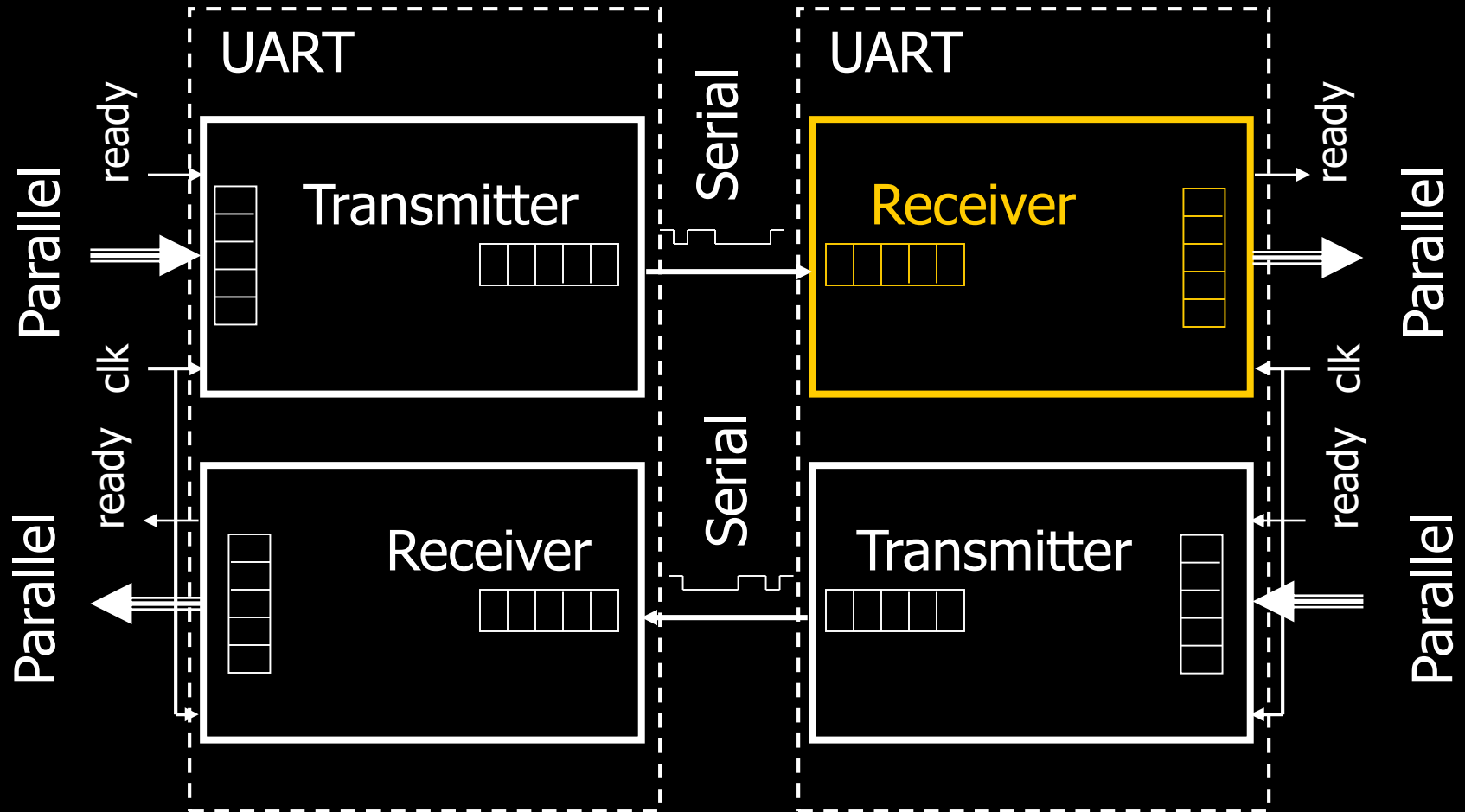


What makes it Asynchronous?

- Separate clock for sender & receiver
 - thus, incoming data not synchronized to local clock
- Serial input data can start at any time
- Only one guarantee regarding timing:
 - Duration of each bit will be uniform, within some tolerance


Serial Data Transmission

 (note: a wide range of transmission rates are possible)



What is the data value here? Assume LSB first, high=1/low=0
(stop bit omitted)

 
a. 11011010 b. 10110100 c. 00011101 d. 01011011



What is the data value here? Assume LSB first, high=1/low=0
(stop bit omitted)

Detecting a start bit

 - Start Bit for your UART is logic '0'
- Receiver Block must detect '1' to '0' transition, WITHOUT using *negedge* property.
- Start Bit can, and will arrive asynchronously (at any point in the SYSTEM CLOCK period).




What combinational logic function is required to produce active high output when falling edge is detected?

Can this circuit also serve as a synchronizer?


How do you read in serial data?

A shift register

 


How do you send serial data?


A shift register

 


Shift Operation

 


Shift Operation

 


Shift Operation

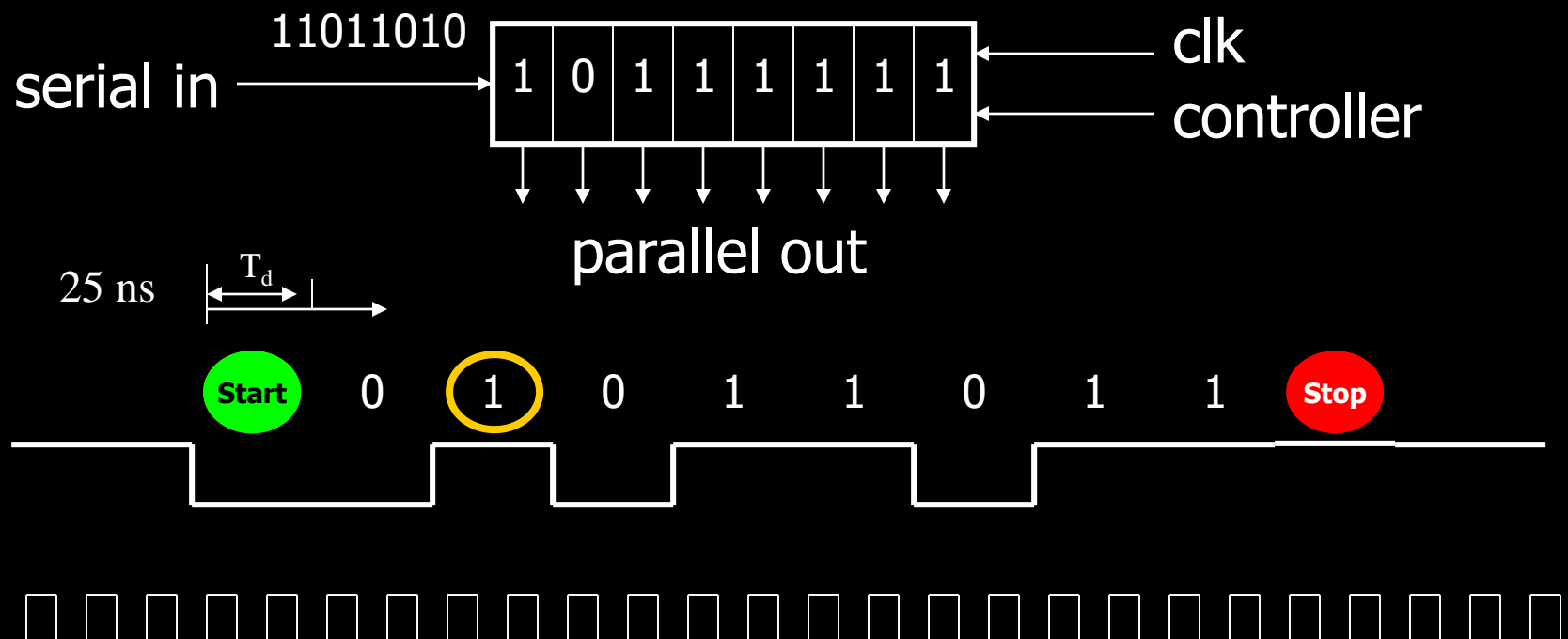

Shift Operation

 



Shift Operation

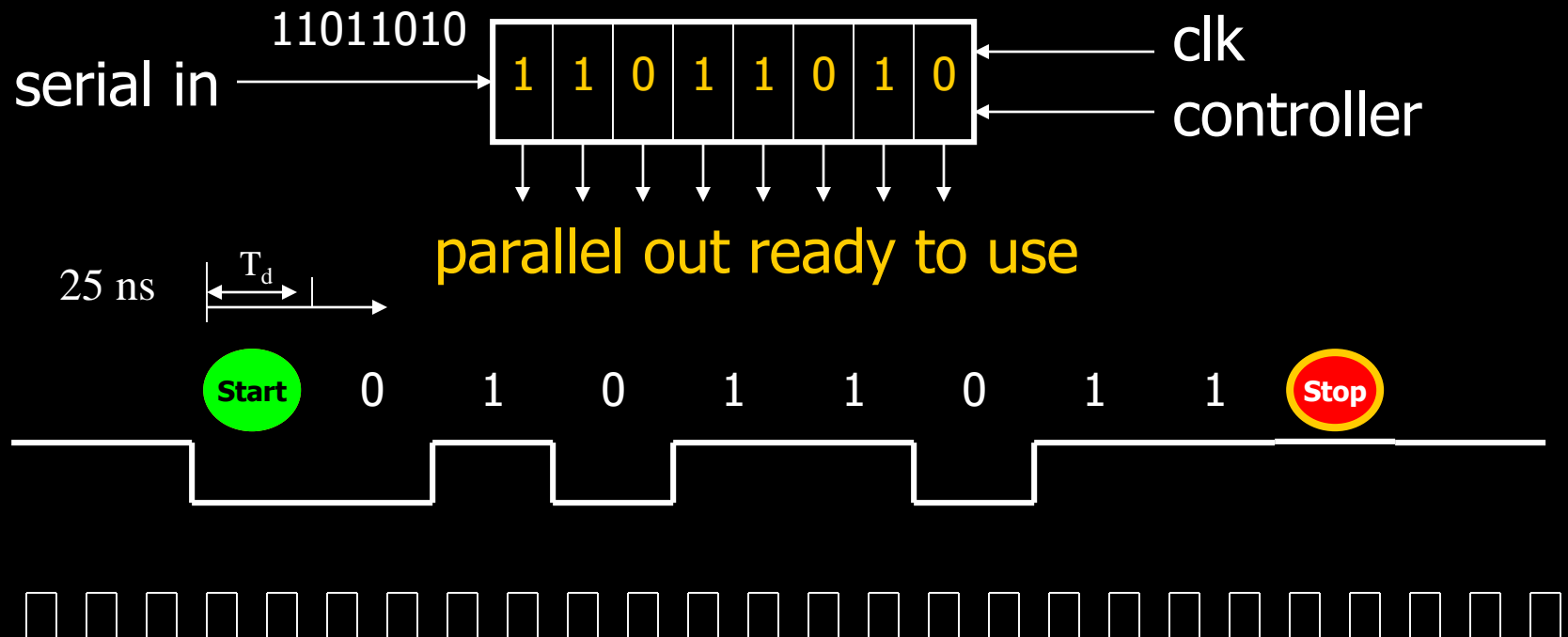



How should bits be shifted?

- One bit per system clock cycle?
 - Not unless system clock is synchronized to data and matches data rate
- We will use a control input to trigger shifting
 - You will create a timer block to generate pulses at the right time


You decide when to shift

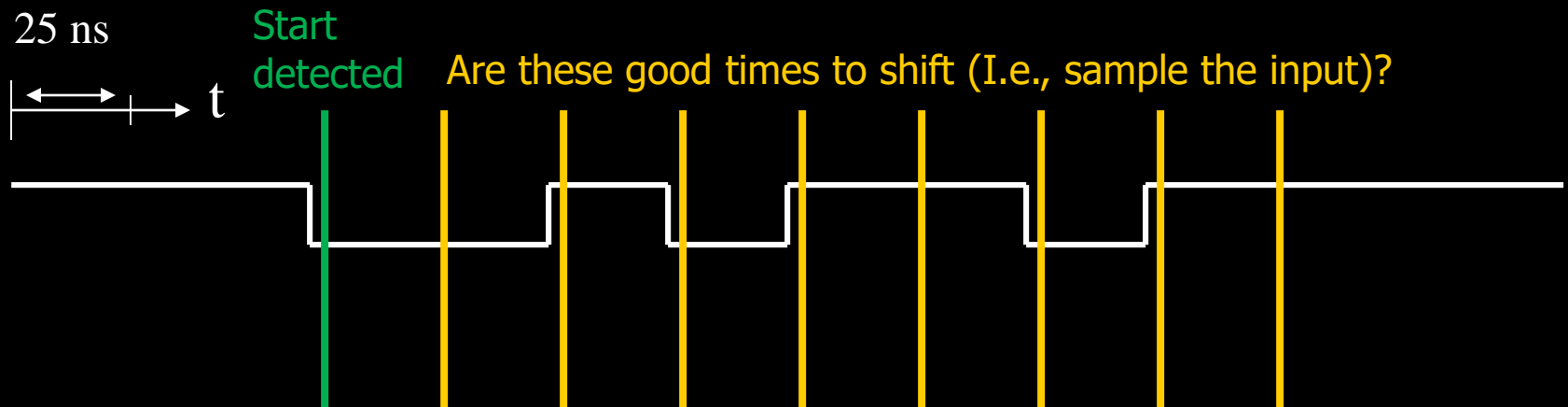 

You decide when to shift

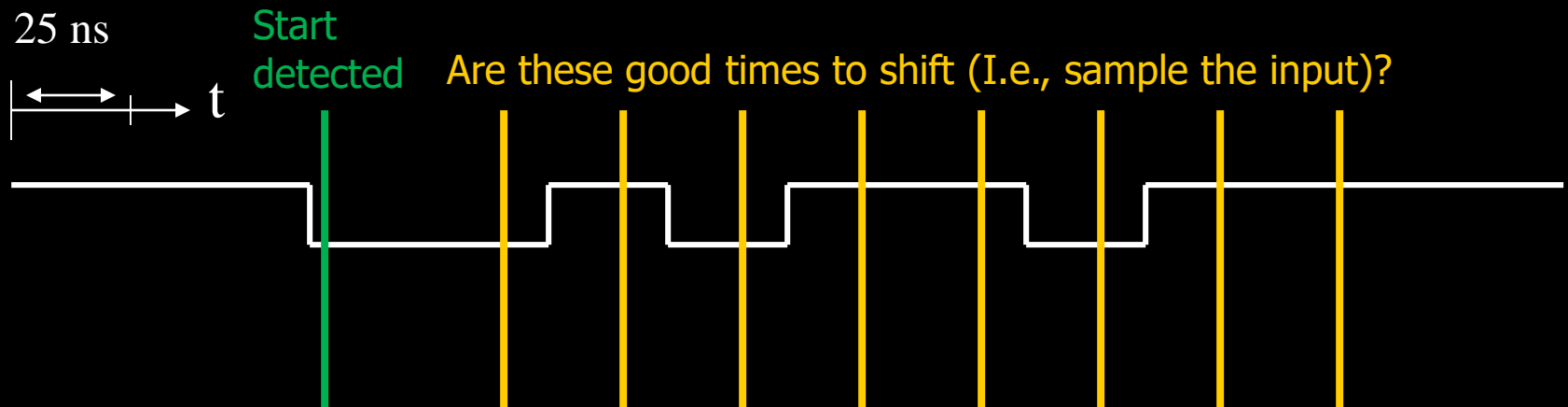 

UART Receive Architecture

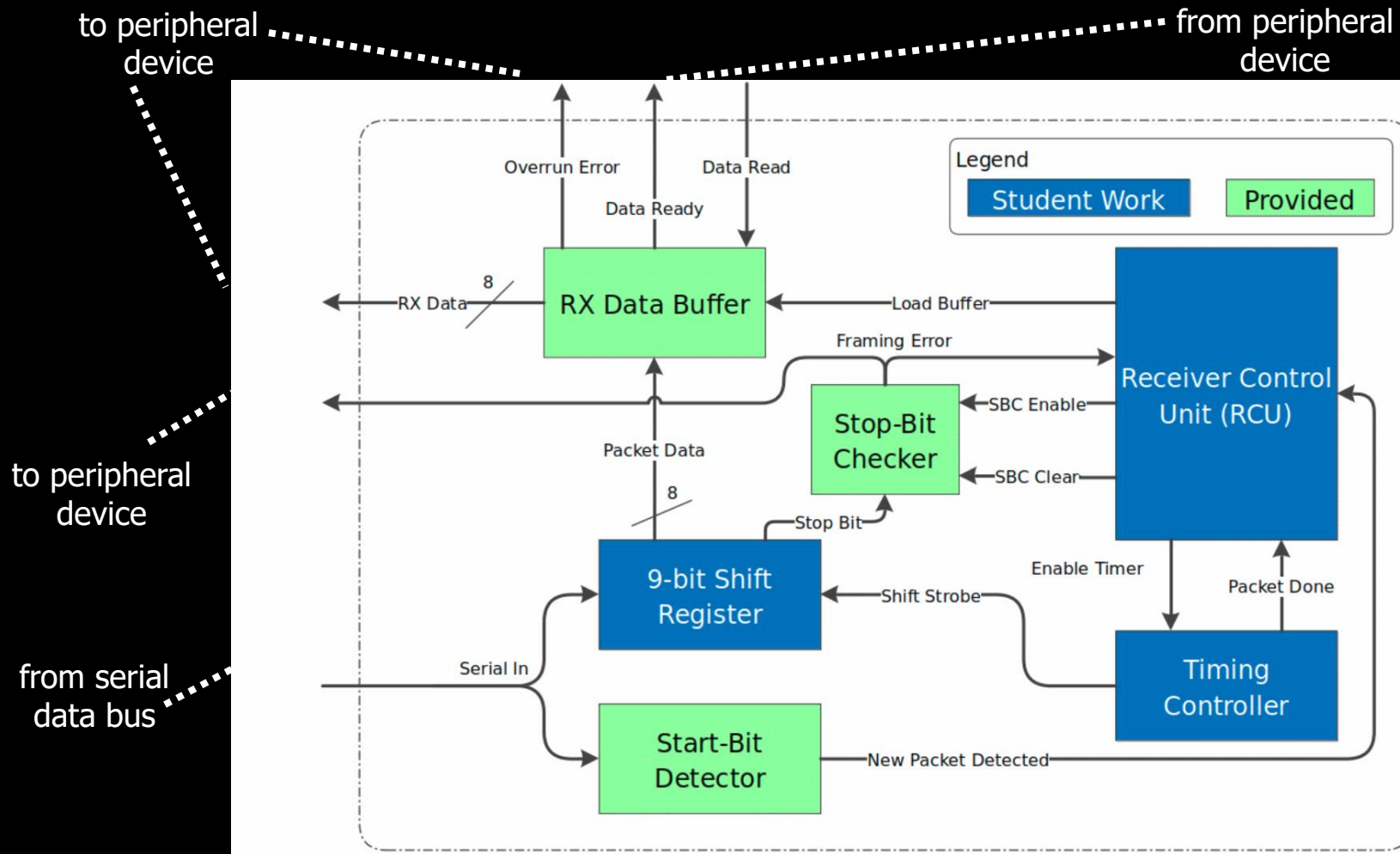

Sequence of Operation

1. Input line is idle ('1'), receiver is waiting for start bit
2. Start bit (1->0 transition is detected)
3. Control unit enables timer
4. Timer enables shift register at appropriate clock cycles to sample each bit and stop bit
5. Timer signals control unit that all bits have been sampled
6. Control unit enables stop-bit checker.
 1. If there is an error, framing_error is asserted and receiver goes back to wait state

Sequence of Operation Continued

7. Control unit enables receiver buffer register to load data from shift register.
8. Peripheral device (or your test bench) should read data from the device and assert the `data_read` signal to inform the buffer that the data has been read

Things you should check:

- Have you checked for a varying data packet speed?
- Does your reset TRULY reset all flip-flops?
- Does your design meet the minimum input specs?
- Are your makefile variables filled in

More food for thought:

- Exhaustive testing is unnecessary
- Test for corner cases
- Ensure that all signals (input, output, and internal) change during your test bench
- Make sure your design can escape error conditions (without using the reset)

Making Debugging Easier

- Set the path length on signal names in wave view
- Saving/making .do files to setup waveforms
 - Make separate .do files for each subblock's signals
 - Save/set the signals you need for each subblock
 - Save/set the radix and formatting for signals
- Only have signals you need to focus on in the waveforms window

Recommended TB Expansions

- Create a new task to encapsulate the code need to run a test case
 - Use conditionals to allow the task to handle test cases with bad stop bits, and other error cases
- Add Test Cases for checking that all of your resets are working
 - including resetting the design while it's receiving a packet
- Ask a TA if you have questions about the testbench